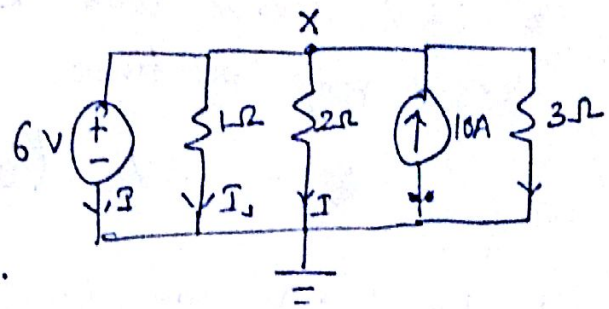


1) This is a very straight forward question and requires a basic knowledge of concepts.

V at Node X = 6V
∴ there is a voltage source.



$$\begin{aligned}\therefore I_{1\Omega} &= \frac{6}{1} = 6A \\ I_{2\Omega} &= \frac{6}{2} = 3A \\ I_{3\Omega} &= \frac{6}{3} = 2A\end{aligned}$$

By KCL $I_{6V} = 10 - (6 + 3 + 2) = -1A$

$$\therefore P_{1\Omega} = I_{1\Omega}^2 R = 36W$$

$$P_{2\Omega} = I_{2\Omega}^2 R = 18W$$

$$P_{3\Omega} = I_{3\Omega}^2 R = 12W$$

$$P_{10A} = V \cdot I = -6 \times 10 = -60W$$

$$P_{6V} = V \cdot I = 6 \times -1 = -6W$$

$$\text{Total power} = 36 + 12 + 18 - 60 - 6 = 0 \checkmark$$

2) Our aim is to find $P_{2\Omega}$ using KCL and not to solve the complete circuit.


KCL at X.

$$I = 5 - 2 = 3A$$

$$\therefore P_{2\Omega} = 3^2 \times 2 = 18W$$

That's it


No more time wasting.

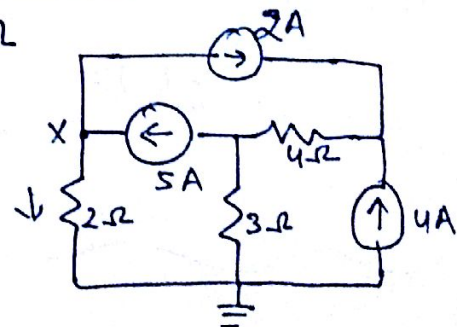

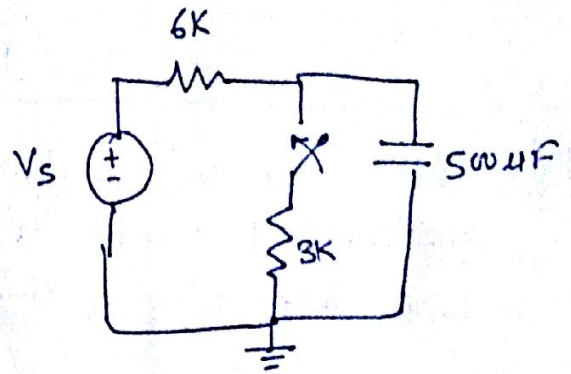3) → for $t < 0$

The capacitor has been connected to 12V source with 6k resistor for a very long time.

$$\therefore V_C = 12V \quad (\text{for } t < 0)$$



→ for $t > 0$ and $t < 10$

$V_S = 24V$ and thus V_C would increase and reach 24V eventually.

$$V_C(t) = V_C(\infty) + [V_C(0) - V_C(\infty)]e^{-t/\tau}$$

$$\tau = RC = 6 \times 10^3 \times 500 \times 10^{-6} = 3$$

$$\therefore V_C(t) = 24 - 12e^{-t/3}$$

→ For $t > 10$

$$V_C(10) = 24 - 12e^{-10/3} = 23.54V$$

Since the switch is closed now and thus V_C is parallel to V_{3k} and both should be equal.

$\therefore V_C$ would discharge to 8V with $\tau = 3k \times 500\mu F = 1.5$

$$\therefore V_C(t) = 8 + (23.54 - 8)e^{-\frac{t-10}{1.5}} \quad \text{exp}\left(\frac{t-10}{1.5}\right)$$

~~$8 + 15.54e^{-\frac{t-10}{1.5}}$~~

$8 + 15.54e^{-\frac{(t-10)}{1.5}} \text{ V}$

Be Careful about $t-10$


4)

4)

Before $t=0$

$$i(0) = 0$$

$$V_C(0) = 10V$$

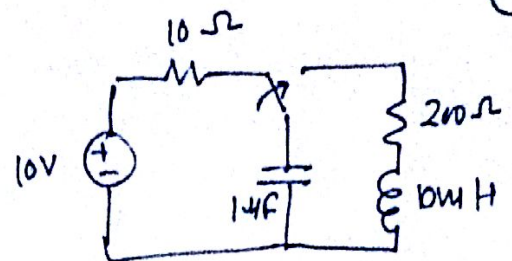

After $t=0$ The circuit becomes a source free circuit

By KVL

$$\frac{1}{C} \int i dt + L \frac{di}{dt} + Ri = 0$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

$$\rho = \frac{R}{2\sqrt{LC}}, \quad \omega_n = \frac{1}{\sqrt{LC}}$$

$$= 1$$

$$\omega_n = \frac{1}{\sqrt{10^{-2} \times 10^{-6}}} = 100$$

assuming e^{st} = solution.

$$\therefore s^2 + 2\rho\omega_n s + \omega_n^2 = 0$$

$$s = -100$$

$$\text{Solution is } Ae^{st} + Bt e^{st}$$

$$= Ae^{-100t} + Bt e^{-100t}$$

at $t=0$

$$i(0) = 0 = Ae^{-100 \times 0} + B \cdot 0 \cdot e^{-100 \cdot 0}$$


$$\Rightarrow A = 0$$

$$V = -(V_R + V_L)$$

$$= -\left[Ri + L \frac{di}{dt}\right] =$$

$$\text{at } t=0 \quad 10 = -\left[R i(0) + L \frac{di(0)}{dt}\right]$$

(3)

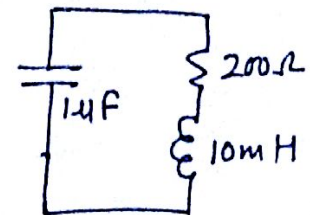

$$i(t) = Ae^{-100t} + tBe^{-100t}$$

$$10 = -0 + B \left[-100A - 100B \right]$$

$$= B = \frac{1}{10}$$

$$\therefore i(t) = 0.1e^{-100t} + \frac{1}{10}te^{-100t}$$

I might have made slight mistake in this last step.
 please cross check this step.

5) Currently this topic is not covered in any
 of the sections.

Best Wishes.