

**Date:** 27th November, 2018

**Time:** 3 hours

Max. Marks (Part - A): **10**

Max. Marks (Part - B): **50**

**Instructions:**


1. This question paper has total **6** pages, including this page.
2. This question paper consists of **Part A** (10 marks) and **Part B** (50 marks). There is no negative marking.
3. Part - A has 8 multiple choice questions. **All questions are compulsory.**
4. Part - B has 6 questions of 10 marks each. **Attempt any 5 questions.**
5. Start each answer on a fresh page and **highlight** your answers.

**Part - A (Quiz 4)**

**NO credit will be given if answer is not correct for Part - A**

**MCQ 1)** A logic circuit consists of two 2X4 decoders as shown below:

**[2]**

 

The outputs of the decoders are as follows:

$D_0 = 1$  when  $A_0 = 0, A_1 = 0$        $D_1 = 1$  when  $A_0 = 1, A_1 = 0$   
 $D_2 = 1$  when  $A_0 = 0, A_1 = 1$        $D_3 = 1$  when  $A_0 = 1, A_1 = 1$

The value of  $f(x,y,z)$  is:

- [A] 0                                      [B]  $z$                                       [C]  $\bar{z}$                                       [D] 1

**Solution: D**

**MCQ 2)** What is one disadvantage of an S-R flip-flop?

**[1]**

- [A] It has no enable input.      [B] It has an invalid state.  
[C] It has no clock input.      [D] Possibility of race-around condition when both inputs are high.

**Solution: B**

**MCQ 3)** A group of 4 bits is known as

- [A] a nibble                              [B] a byte                              [C] a q-bit                              [D] a quad                              **[1]**

**Solution: A**

**MCQ 4)** Let  $(A2C)_{16} = (X)_8$ . Then X is given by:

**[1]**

- [A] 7054                              [B] 6054                              [C] 5154                              [D] 5054

**Solution: D**

**MCQ 5)** How many NOR gates are required to realise a AND gate?

[A] 2

[B] 3

[C] 4

[D] 5

[1]

**Solution: B**

**MCQ 6)** How many select lines are contained in a multiplexer with 1024 inputs and one output?

[A] 512

[B] 258

[C] 64

[D] 10

[1]

**Solution: D**

**MCQ 7)** If functions  $W, X, Y$  and  $Z$  are as follows:

$$W = R + \overline{P}Q + \overline{R}S$$

$$X = PQ\overline{R}\overline{S} + \overline{P}\overline{Q}\overline{R}\overline{S} + P\overline{Q}\overline{R}\overline{S}$$

$$Y = RS + \overline{P}R + P\overline{Q} + \overline{P}\overline{Q}$$

$$Z = R + S + PQ + \overline{P}\overline{Q}\overline{R} + P\overline{Q}\overline{S}$$

Then

[A]  $W = Z, X = \overline{Z}$

[B]  $W = Z, X = Y$


[C]  $W = Y$

[D]  $W = Y = \overline{Z}$

[2]

 **Solution: A**

**MCQ 8)** The symbols on the flip-flop shown below indicate:



[1]

[A] triggering takes place on the negative-going edge of the CLK pulse

[B] triggering takes place on the positive-going edge of the CLK pulse

[C] triggering can take place anytime during the HIGH level of the CLK waveform

[D] triggering can take place anytime during the LOW level of the CLK waveform

**Solution: A**

## Part - B (Main Exam)

**Q1) a)** A series resonant circuit has  $L = 1\text{mH}$  and  $C = 10\mu\text{F}$ . Calculate the value of  $R$  required if the bandwidth  $BW = 15.9\text{ Hz}$ . 74/9

[2]

**Solution:**

$$BW = \frac{R}{L}$$


1

$$\Rightarrow \frac{R}{1 \times 10^{-3}} = 15.9 \times 2\pi = 0.1\Omega$$

1

b) Twelve  $6\Omega$  resistors are placed along each edge of a cube. Calculate the equivalent resistance between any two diagonally opposite corner points. [2]

**Solution:**

 

From the above image, due to symmetry and all resistances being same (6 ohm), current  $i$  will split as shown above.

Total current between 2 diagonally opposite edges will be –

$$i_{eq} = i/3 + i/6 + i/3 = 5i/6$$

$$V = i_{eq}R = 5i/6 \times 6 = 5i$$

$$V_{eq} = R_{eq} \times i$$

$$R_{eq} = 5\Omega$$

NO partial credit

**Note: Students who have correctly and fully solved the problem assuming  $R_{eq}$  for face diagonal instead of body diagonal, will get full credit.**

c) For the circuit given below, find  $i_1$ :

 


Figure 1.c

[3]

**Solution:**

$$v_x = 500i_1$$

$$v_y = 400(i_1 - 0.001v_x) = 400(i_1 - 0.5i_1) = 200i_1$$

$$180 = 500i_1 + 100(i_1 - 0.6) + 200i_1 + 100(i_1 + 0.005v_y)$$

$$180 = 900i_1 - 60 + 100 \times 0.005 \times 200i_1$$

$$i_1 = 0.12 \text{ A}$$

1.5

1.5

d) For the circuit given below, find  $i(t)$ :

 


Figure 1.d

[3]


**Solution:**

$$V_a = \frac{\frac{10 \angle 0}{1}}{\frac{1}{1} + \frac{1}{-j2} + \frac{1}{4 + j8}} = \frac{10 \angle 0}{1.05 + j0.4} \text{ V}$$

1.5

$$I = \frac{V_a}{4 + j8} = \frac{10 \angle 0}{1 + j10} = 1 \angle -84.23^\circ \text{ A}$$

1.5

 

$$i(t) = \cos(2t - 84.23^\circ) \text{ A}$$

Q2) a) Calculate the Thevenin's equivalent resistance  $R_{Th}$  for the following circuit:

[3]


 


Figure 2.a
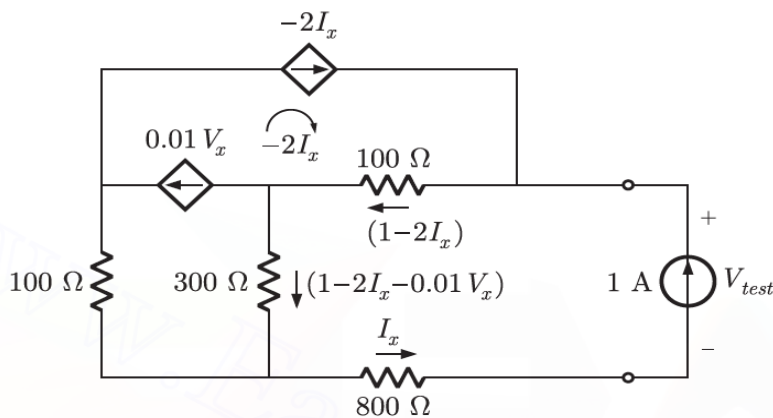
### Solution:

Writing currents into  $100 \Omega$  and  $300 \Omega$  resistors by using KCL as shown in figure.



$$I_x = 1 \text{ A}, V_x = V_{test}$$

Writing mesh equation for bottom right mesh.

$$V_{test} = 100(1 - 2I_x) + 300(1 - 2I_x - 0.01 V_x) + 800 = 100 \text{ V}$$

1.5

$$R_{Th} = \frac{V_{test}}{1} = 100 \Omega$$

1.5

b) For the network shown below:

[2]

 


Figure 2.b

$R_L$	10 kΩ	30 kΩ
$P$	3.6 mW	4.8 mW

Table 2.b

The power absorbed by load resistor  $R_L$  is shown in the table 2.b above. At what value of  $R_L$  would the power absorbed be maximum?

**Solution:**

For  $R_L = 10 \text{ k}\Omega$ ,  $V_{ab1} = \sqrt{10\text{k} \times 3.6\text{m}} = 6 \text{ V}$

For  $R_L = 30 \text{ k}\Omega$ ,  $V_{ab2} = \sqrt{30\text{k} \times 4.8\text{m}} = 12 \text{ V}$

$$V_{ab1} = \frac{10}{10 + R_{Th}} V_{Th} = 6 \quad \dots(i)$$

$$V_{ab2} = \frac{30}{30 + R_{Th}} V_{Th} = 12 \quad \dots(ii)$$

Dividing equation (i) and (ii), we get  $R_{Th} = 30 \text{ k}\Omega$ . Maximum power will be transferred when  $R_L = R_{Th} = 30 \text{ k}\Omega$ .

c) In the following second order circuit, the switch is moved from position a to b at  $t = 0$ .

Find  $i_L(t)$  for  $t > 0$ .

**[3]**

 


Figure 2.c

**Solution:**

$$v_C(0) = 0, \quad i_L(0) = \frac{4 \times 6}{6 + 2} = 3$$

$$0.02 \frac{dv_C(0)}{dt} = i_L(0) = 3 \Rightarrow \frac{dv_C(0)}{dt} = 150$$

$$\alpha = \frac{6 + 14}{2 \times 2} = 5, \quad \omega_o = \frac{1}{\sqrt{2 \times 0.02}} = 5$$

$$\alpha = \omega_o \text{ critically damped}$$

$$v(t) = 12 + (A + Bt)e^{-5t}$$

$$0 = 12 + A, \quad 150 = -5A + B \Rightarrow A = -12, \quad B = 90$$

$$v(t) = 12 + (90t - 12)e^{-5t}$$

$$i_L(t) = 0.02(-5)e^{-5t}(90t - 12) + 0.02(90)e^{-5t} = (3 - 9t)e^{-5t}$$

d) Calculate  $R_{eq}$ :


 


Figure 2.d

[2]

**Solution:**

 


**Converting Delta to Star –**


$$R_1 = 24/12 = 2$$

$$R_2 = 8/12 = 2/3$$


$$R_3 = 12/12 = 1$$

 

which equals to :

 

which equals to :

 

**= 9Ω**

NO partial credit

**Q3) a)** For the following circuit, derive the expression for transfer function  $H(\omega)$  :

**[2]**

 


Figure 3.a

**Solution:**

Applying Superposition theorem:

$$v_0 = \frac{v_1 \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \left[ 1 + \frac{R_1}{R_1} \right] + v_2 [-1]$$

1

But,  $v_2 = v_1$

$$v_0 = v_1 \left[ \frac{2}{1 + j\omega RC} - 1 \right]$$

$$\frac{v_0}{v_1} = \frac{2 - 1 - j\omega RC}{1 + j\omega RC}$$

$$\frac{v_0}{v_1} = \frac{1 - j\omega RC}{1 + j\omega RC}$$

$$= H(\omega)$$

1




b) Draw the Gain plot for  $H(\omega)$  obtained in Q3 a.

[2]

**Solution:**

$$\frac{v_o}{v_i} = H(j\omega) = \frac{1 - j\omega RC}{1 + j\omega RC}, \quad |H(j\omega)| = \frac{\sqrt{1 + (\omega RC)^2}}{\sqrt{1 + (\omega RC)^2}} = 1$$

1

 

1

c) For the opamp circuit given below, derive the expression for differential gain,  $G = \frac{V_o}{V_2 - V_1}$ .

[3]

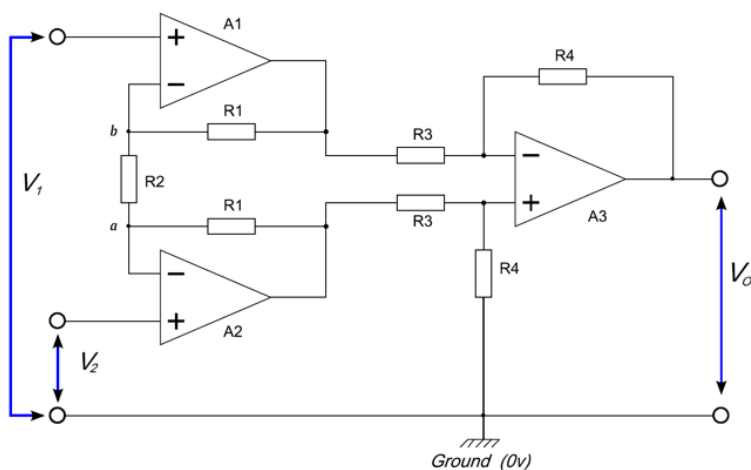


Figure 3.c

**Solution:** Derivation of Instrumentation Amplifier.

$$\frac{R_4}{R_3} \left[ 1 + \frac{2R_1}{R_2} \right]$$

2

1 mark will be given based on attempt

d) For the circuit given below:

[3]

 


Figure 3.d.i


 


Figure 3.d.ii

Draw the output  $v_o(t)$  waveform for the input  $v_i(t)$  given above, if  $R = 4M\Omega$  and  $C = 2\mu F$ .

**Solution:**

 

Stage 1


Stage 2

Stage 2 is unity gain Inverting amplifier.

Let,  $V_a = V_b = V$

At node a,  $\frac{0-V}{R} = \frac{V-V_0}{R}$

$V = V_0/2$  ----- (i)

 

Stage 1 : At node b,

$$\frac{V_i - V}{R} = \frac{V - V_0}{R} + C \frac{dV}{dt}$$

$$V_i = 2V - V_0 + RC \frac{dV}{dt} \quad \text{----- (ii)}$$

Combining (i) and (ii)

$$V_i = V_0 - V_0 + \frac{RC}{2} \frac{dV_0}{dt}$$

$$\text{Or, } V_0 = \frac{2}{RC} \int V_i dt$$

Thus, Stage 1 is functioning like a non-inverting integrator.

Stage 1 is cascaded with Stage 2, thus, the complete circuit functions as an inverting integrator.

$$\text{Therefore, } V_0 = - \frac{2}{RC} \int V_i dt$$

1

Waveform representation:

$$V_0 = - \frac{2}{RC} \int V_i dt = - \frac{1}{4} \int V_i dt$$


$$\text{For } 0 < t < 1, \quad V_i = 20, V_0 = - \frac{1}{4} \int_0^t 20 dt = -5t \text{ mV}$$

$$\text{For } 1 < t < 2, \quad V_i = 10, V_0 = - \frac{1}{4} \int_1^t 10 dt + V(1) = -2.5t - 2.5 \text{ mV}$$

1

Similarly, continue for other timestamps.

Thus,  $V_0(t)$  is represented as:

 

1

**Q4) a)** For the opamp amplifier circuit below, calculate the value of  $R$  so that the closed loop gain  $A_v = v_o/v_i = -10$ .

[2]


 


Figure 4.a

**Solution:**

 

Using virtual short,  $V_x = 0$

Applying KCL at node a,

$$\frac{V_x - V_i}{100K} = \frac{V_y - V_x}{R} \Rightarrow \frac{-V_i}{100K} = \frac{V_y}{R} \quad \text{----- (i)}$$

Nodal analysis at node b,

$$\frac{V_y - V_x}{R} + \frac{V_y}{100K} + \frac{V_y - V_o}{100K} = 0 \quad \text{As } v_x = 0;$$

$$\frac{100K}{R} V_y + V_y + V_y - V_o = 0 \Rightarrow V_o = \left(2 + \frac{100K}{R}\right) V_y \quad \text{----- (ii)}$$

1

Taking ratios of eq. i and ii

$$\frac{V_o}{V_i} (-100K) = \frac{\left(2 + \frac{100K}{R}\right) V_y}{\frac{V_y}{R}}$$

$$\frac{V_o}{V_i} (-100K) = 2R + 100K$$

But,  $V_o/V_i = -10$  (from given question)

$$\therefore 1000 K = 2R + 100K$$

$$\Rightarrow 2R = 900 k\Omega$$

$$\Rightarrow \mathbf{R = 450 k\Omega}$$

1

**b)** Derive the transfer function  $H(\omega)$  for the following circuit. Identify the type of filter.

**[3]**

 


Figure 4.b

**Solution:**

$H(\omega) = V_o/V_i = -R_f/R_i$  as this is inverting mode

$$R_f = R_2 \parallel \frac{1}{j\omega C} = \frac{R_2}{j\omega C(R_2 + \frac{1}{j\omega C})} = \frac{R_2}{1 + j\omega R_2 C}$$

$$R_i = R_1 + j\omega L$$

$$H(\omega) = -\frac{R_2}{(1 + j\omega R_2 C)(R_1 + j\omega L)} = \frac{-R_2}{R_1} \left[ \frac{1}{(1 + j\omega \frac{L}{R_1})(1 + j\omega R_2 C)} \right]$$

2

At  $\omega=0$ ,  $|H(\omega)| = -R_2/R_1$  ----- passband or DC gain

At  $\omega = \infty$ ,  $|H(\omega)| = 0$

Filter behaves as a low-pass filter

1

**c)** Design a 4-bit BCD to Excess – 3 (XS-3) code converter. Use sum of products (minterms) format.

**[3]**


**Solution:**

Let  $A, B, C$ , and  $D$  be the bits representing the binary numbers, where  $D$  is the LSB and  $A$  is the MSB, and let  $w, x, y$ , and  $z$  be the bits representing XS-3 code of the binary numbers, where  $z$  is the LSB and  $w$  is the MSB. The truth table for the conversion is given below. The X's mark don't care conditions.

1

BCD(8421)				Excess-3			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

 To find the corresponding digital circuit, we will use the K-Map technique for each of the Excess-3 code bits as output with all of the bits of the BCD number as input.




1.5

Corresponding minimized Boolean expressions for Excess-3 code bits –

$$\begin{aligned}w &= A + BC + BD \\x &= B'C + B'D + BC'D' \\y &= CD + C'D' \\z &= D'\end{aligned}$$

The corresponding digital circuit-

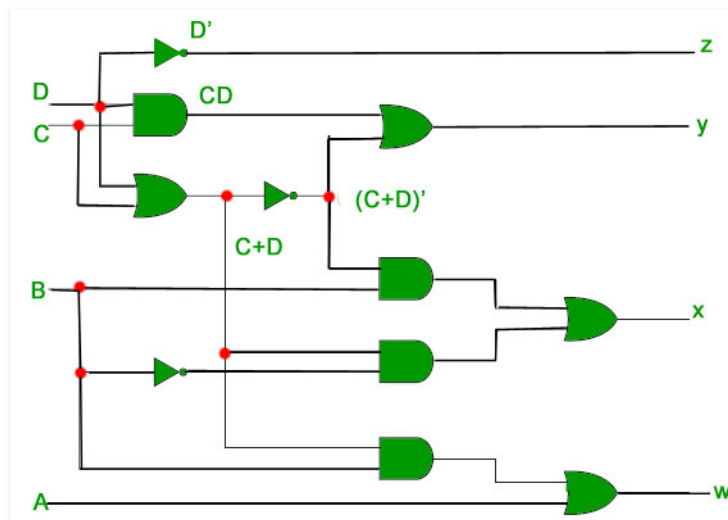

0.5

d) Verify if the Boolean expression  $(A + \overline{B})(\overline{A} + B) = \overline{A}\overline{B} + AB$  is true, using truth tables.

[2]

**Solution:**

A	B	$\overline{A}$	$\overline{B}$	$(A + \overline{B})$	$(\overline{A} + B)$	$(A + \overline{B})(\overline{A} + B)$	$AB$	$\overline{A}\overline{B}$	$\overline{A}\overline{B} + AB$
0	0	1	1	1	1	1	0	1	1
0	1	1	0	0	1	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	1	1	1	0	1

Since, LHS  $\neq$  RHS, the given Boolean expression is FALSE.

No partial credit

**Q5) a)** A lawn sprinkling system is controlled automatically by certain combinations of the following variables: 112

[3]

- Season ( $S = 1$  if summer,  $S = 0$  otherwise)
- Moisture content of soil ( $M = 1$  if high,  $M = 0$  if low)
- Outside temperature ( $T = 1$  if high,  $T = 0$  if low)
- Outside humidity ( $H = 1$  if high,  $H = 0$  if low)

The sprinkler should be turned on under any of the following conditions:

- The moisture content is low in winter.
- Temperature is high and moisture content is low in summer.
- Temperature and humidity both are high in summer.
- Temperature and moisture content both are low in summer.
- Temperature is high and humidity is low.

Use a K-map to find the simplest logic expression (both sum of products [minterm] and product of sums [maxterm]) involving variables  $S, M, T, H$  for turning on the sprinkler system. Draw the logic circuit using only NAND gates.

### Solution:

The given circumstances 1,2,3,4 and 5 are expressed in terms of the defined variables  $S, M, T$  and  $H$  as  $\bar{M}\bar{S}, T\bar{M}S, THS, \bar{T}\bar{M}S$  and  $T\bar{H}$ , respectively.

The Boolean expression is

$$\bar{S}\bar{M} + \bar{S}MT + STH + \bar{S}\bar{M}\bar{T} + T\bar{H}$$

$$= 00XX + 101X + 1X11 + 100X + XX10$$

1


The expression in terms of minterms and maxterms are

$$\sum m(0, 1, 2, 3, 6, 8, 9, 10, 11, 14, 15)$$

$$\prod M(4, 5, 7, 12, 13)$$

 0.5

Both the SOP and POS forms give same minimum.




1.5



b) Implement an OR gate using NAND gates

[2]

**Solution:**

 

c) Solve the following problems:

[5]

- Convert  $(163.875)_{10}$  to binary
- Perform subtraction  $100-110000$  using 2's complement method.
- Convert  $(110101.101010)_2$  to octal.
- Convert  $(3A9E.B0D)_{16}$  to binary.
- In what radix (base) number system will  $\sqrt{41} = 5$ ?

**Solution:**

- $(163.875)_{10} = (10100011.111)_2$
- $100-110000 = 1010100$   
Since there is no carry and MSB is 1, it's a negative number. Taking 2's complement and putting a minus sign, we get  $-0101100 = -44$
- $(110101.101010)_2 = (65.52)_8$
- $(3A9E.B0D)_{16} = (11101010011110.101100001101)_2$
- Radix will be 6

NO partial credit, 1 mark each

**Q6) a)** Implement a J-K latch using NAND gates. Write its truth-table and explain any issue with the J-K latch using timing diagram. Suggest any two solutions to solve the issue.

[2]

**Solution:** Circuit – 0.5 marks  
Truth table – 0.5 marks  
Race around condition using time diagram – 0.5 marks  
Solutions (use edge triggered or master-slave) – 0.5 marks

**b)** Implement a master-slave JK flip-flop using only NAND gates. Write its truth table and draw timing diagram showing at least 6 clock pulses.

[3]


**Solution:** Circuit – 1 mark  
Truth table – 0.5 marks  
Timing diagram – 1.5 marks

c) Implement a full subtractor using only 2-input NOR gates.

[3]

**Solution:**

Minuend (A)	Subtrahend (B)	Borrow In ( $B_{in}$ )	Difference (D)	Borrow Out ( $B_o$ )
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 

1

$\overline{AB}$	$\overline{B_{in}}$	$B_{in}$
$\overline{AB}$		1
$\overline{AB}$	1	
$AB$		1
$AB$	1	

$$D = \overline{A} \cdot \overline{B} \cdot B_{in} + \overline{A} \cdot B \cdot \overline{B_{in}} + A \cdot \overline{B} \cdot \overline{B_{in}} + A \cdot B \cdot B_{in}$$


$\overline{AB}$	$\overline{B_{in}}$	$B_{in}$
$\overline{AB}$		1
$\overline{AB}$	1	1
$AB$		1
$AB$		

$$B_o = \overline{A} \cdot B + \overline{A} \cdot B_{in} + B \cdot B_{in}$$

1.5

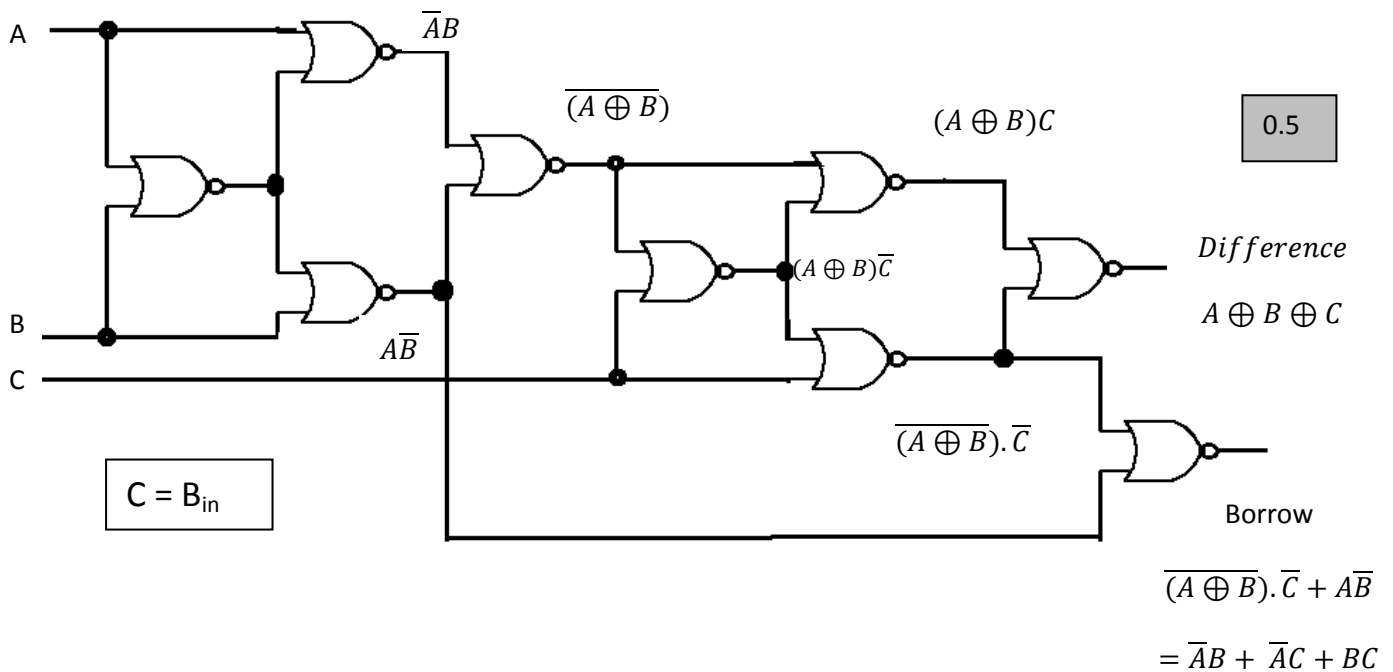**Solving further for D :-**

$$\begin{aligned}
 D &= (\overline{A} \cdot \overline{B} + \overline{A} \cdot B) \cdot \overline{B_{in}} + (\overline{A} \cdot B + A \cdot \overline{B}) \cdot B_{in} \\
 &= (\overline{A} \oplus B) \cdot \overline{B_{in}} + (\overline{A} + B)(A + \overline{B}) \cdot B_{in} \\
 &= (\overline{A} \oplus B) \cdot \overline{B_{in}} + (\overline{A} \cdot \overline{B} + \overline{A} \cdot B + A \cdot \overline{B} + A \cdot B) \cdot B_{in} \\
 &= (\overline{A} \oplus B) \cdot \overline{B_{in}} + (\overline{A} \cdot \overline{B} + \overline{A} \cdot B + A \cdot \overline{B} + A \cdot B) \cdot B_{in} \\
 &= (\overline{A} \oplus B) \cdot \overline{B_{in}} + (\overline{A} \oplus B) \cdot B_{in} \\
 &= (\overline{A} \oplus B \oplus B_{in})
 \end{aligned}$$



**Note:** Students who have cascaded 2 half subtractors will also get full credit provided only NOR gates are used.


**d)** For the expression  $f = \prod M(2,8,9,10,11,12,14)$ , implement the minimal (reduced) expression using only NOR gates.

**[2]**

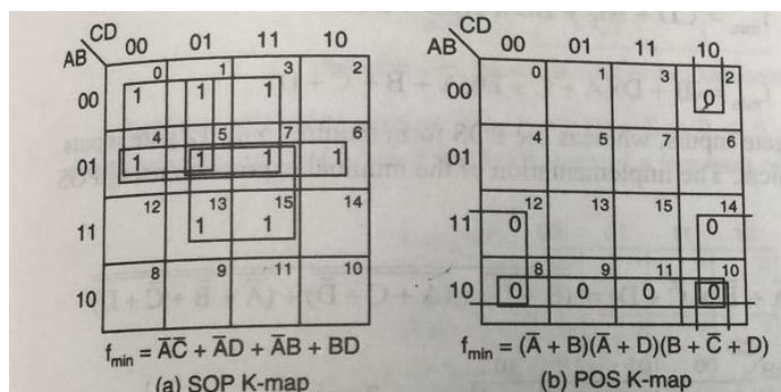**Solution:**

The given expression in the SOP form is  $f = \sum m(0,1,3,4,5,6,7,13,15)$ .

K-map for SOP form, POS form, their reductions and reduced expressions are shown below :



1


It is more economical to implement POS form, which use 10 NOR gates, over SOP form (uses 12 NOR gates).

Reduced POS expression:

$$f_{\min} = (\bar{A} + B)(\bar{A} + D)(B + \bar{C} + D) = \overline{(\bar{A} + B) + (\bar{A} + D) + (B + \bar{C} + D)}$$

0.5

NOR gate implementation:

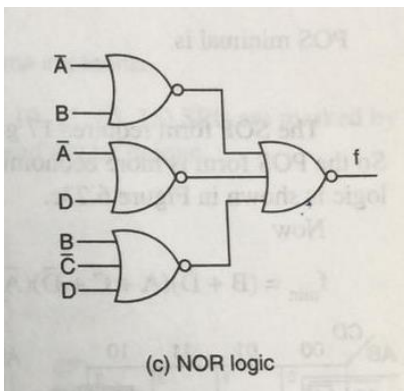

0.5

**END**