

The LNM Institute of Information Technology, Jaipur
Department of Electronics and Communication Engineering
ECE103: Basic Electronics

Mid Term
2017-18 Odd Sem

Degree: B.Tech

Programme: ECE/CCE/CSE/ME

Time: 90 Minutes

Date: 21/09/2017

Maximum Marks: 30

Name:

Section:

Roll No.

Question No.	1	2	3	4	Total
Marks					

Q.1: For the circuit given in figure 1, if, $Z_L = 2 - j4 \Omega$, then calculate the average power (P) consumed by each element in the circuit. Also verify the law of power conservation is followed by this circuit. [7]


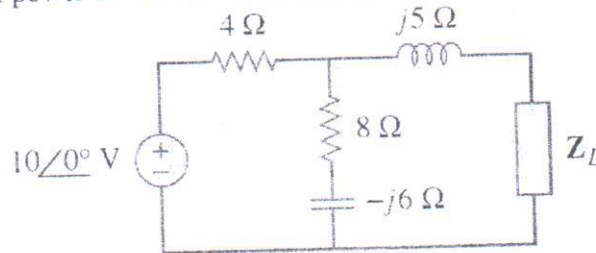
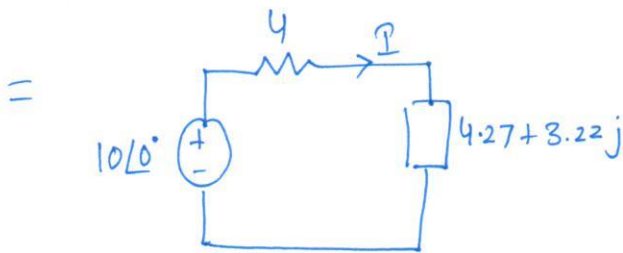


Figure 1.

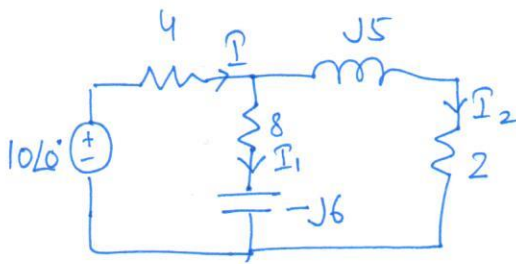

$$\underline{I} = \frac{10\angle 0^\circ}{8.27 + j3.22} = \frac{10\angle 0^\circ}{10.04 \angle -5.7^\circ} = 1.05 - 0.4j \text{ A}$$

$$= 1.12 \angle -20^\circ \text{ A}$$

$$\underline{I}_1 = \frac{5.38 \angle 68.19^\circ}{10.04 \angle -5.7^\circ} \times 1.12 \angle -20^\circ$$

$$= 0.60 \angle 53.7^\circ \text{ A}$$

$$= 0.36 + j0.48 \text{ A}$$

$$\underline{I}_2 = \frac{10 \angle -36^\circ \times 1.12 \angle -20^\circ}{10.04 \angle -5.7^\circ}$$

$$= 1.115 \angle -50.3^\circ = 0.71 + j0.86 \text{ A}$$

$$P_{10V} = -V_e I_e \cos \theta$$

$$= -10 \times 1.12 \cos(20^\circ)$$

$$= -10.52 \text{ W} \quad [1]$$

$$P_{4\Omega} = V I \cos \theta$$

$$= I^2 R \cos(0^\circ)$$

$$= (1.12)^2 \times 4 = 5.02 \text{ W}$$

$$P_{8\Omega} = |I_1|^2 R = (0.6)^2 \times 8 = 2.88 \text{ W} \quad [1]$$

$$P_{2\Omega} = |I_2|^2 R = (1.11)^2 \times 2 = 2.64 \text{ W}$$

$$P_{j5} = V_e I_e \cos \theta$$

$$= (j5)(I_1)(I_2) \cos 90^\circ = 0 \text{ W} \quad [1]$$

$$P_{-j6} = 0 \text{ W}$$

[3]

$$\text{Total Power} = -10.52 + 5.02 + 2.88 + 2.64 = 0$$

1

→ If you assume V_s not to be V_e , then

$$P = \frac{1}{2} V I \cos \theta$$

and all the power values will be half of the calculated values.

Name: _____ Section: _____ Roll No. _____
Q2: Find the Thevenin equivalent of the circuit given below as seen from [4+4]

- (a) Terminals a-b (b) terminals c-d



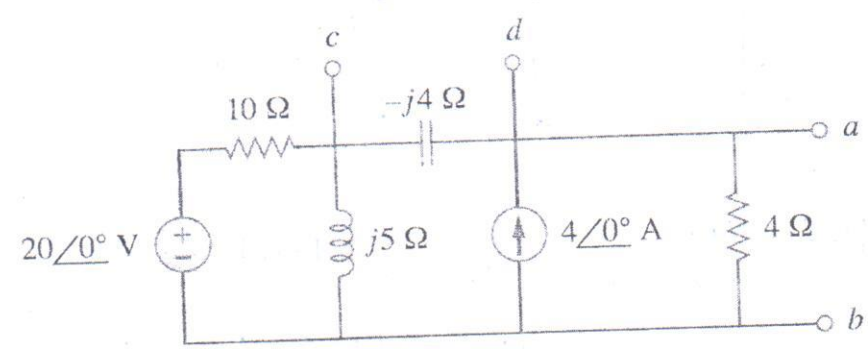


Figure 2

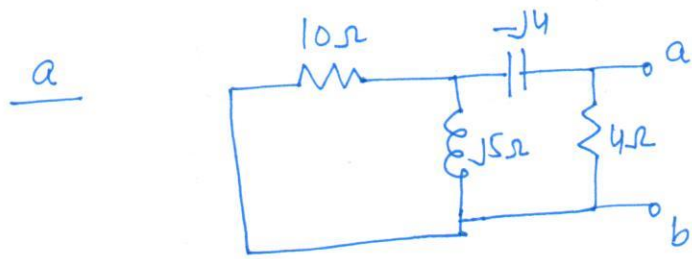

$$R_{TH} = 4 \parallel (-j4 + (10 \parallel j5))$$

$$= 1.33 \Omega \quad [2]$$

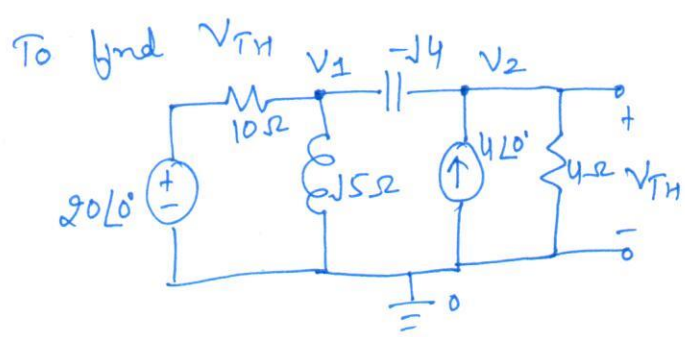

at node V_1

$$\frac{V_1 - 20}{10} - \frac{V_1}{j5} + \frac{V_1 - V_2}{-j4} = 0$$

$$\Rightarrow (1 + j0.5)V_1 - j2.5V_2 = 20 \quad (1)$$

at V_2


$$4 + \frac{V_1 - V_2}{-j4} = \frac{V_2}{4}$$

$$V_1 - (1 - j)V_2 = j16 \quad (11)$$

$$\therefore V_2 = 8 + j5.33$$

$$V_{TH} = V_2 = 8 + j5.33 = 9.615 \angle 3.69^\circ$$

b)

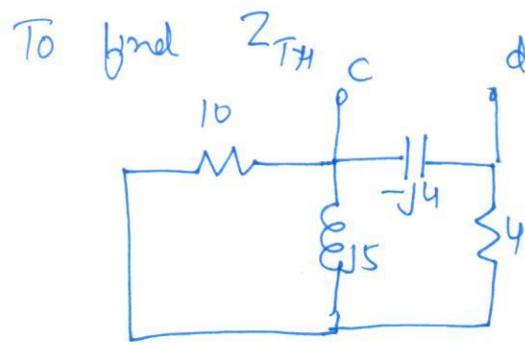

$$Z_{TH} = [(10 \parallel j5) + 4] \parallel (-j4)$$

$$= 2.667 - j4 \Omega$$

[2]

To find V_{TH} .

from part a, we found $V_2 = 8 + j5.33$.

$$V_1 = (1-j)V_2 + j16 = 13.33 + j13.33$$

$$V_{TH} = V_1 - V_2 = 5.33 + j8$$

$$= 9.614 \angle 56.31^\circ$$

[2]

Name:

Section:

Roll No.

Q3: Determine $i(t)$ and $v(t)$ for $t > 0$ in the circuit given below (figure 3), where $v(t)$ is the voltage across capacitor.
[7]


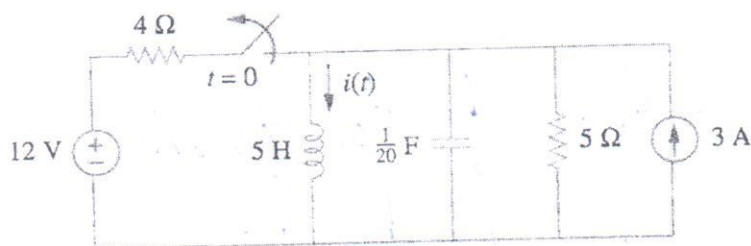


Figure 3

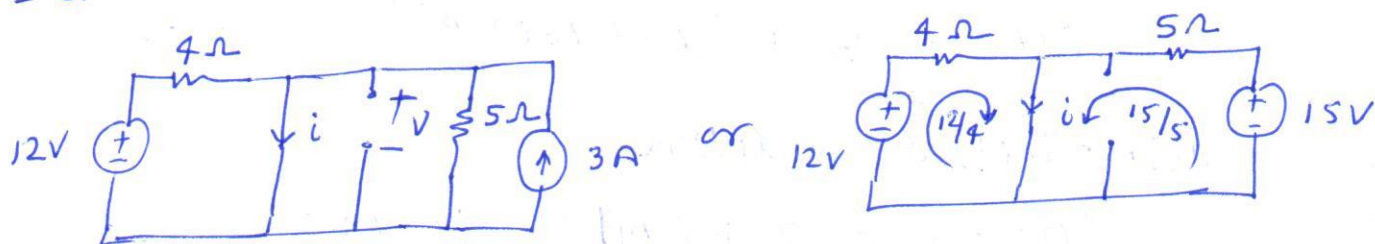
Sol. For $t < 0$ the switch is closed and the ckt becomes



$$\text{Then } i(0) = \frac{12}{4} + \frac{15}{5} = 3 + 3 = 6 \text{ A}$$

$$\text{and } v(0) = L \frac{di(0)}{dt} = 0 \quad (\text{Short ckt})$$

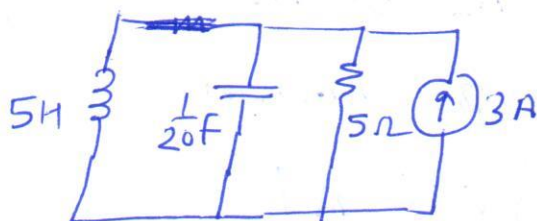For $t > 0$ the switch is open and ckt becomes (before steady state)



Since this is a parallel RLC ckt.

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 5 \times \frac{1}{20}} = 2$$

$$\text{and } \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times \frac{1}{20}}} = 2$$

h


$\alpha = \omega_0$ means Critically damped case of the solution.

Which is in this case of RLC ckt with source

$$i(t) = I_s + (A_1 + A_2 t) e^{-\alpha t}$$

— (1)

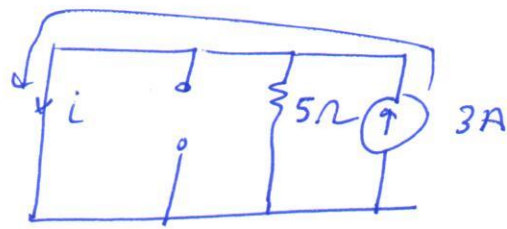Now to calculate I_s (steady state current-)
Ckt becomes.



$$i(\infty) = I_s = 3A$$

then solⁿ becomes.

$$i(t) = 3 + (A_1 + A_2 t) e^{-2t} \quad \text{--- (2)}$$

using initial condition.

$$i(0) = 6 = 3 + (A_1 + 0) \Rightarrow A_1 = 3 \quad \text{--- (1)}$$

and $L \frac{di(0)}{dt} = v(0) = 0 \Rightarrow \frac{di(0)}{dt} = 0$, then from (2)

$$\frac{di(t)}{dt} = 0 - 2(A_1 + A_2 t) e^{-2t} + A_2 e^{-2t} \quad \text{--- (1)}$$

at $t=0$

$$0 = -2(3) + A_2 \Rightarrow A_2 = 6 \quad \text{--- (1)}$$

using $A_1 = 3, A_2 = 6$ (2) becomes

$$i(t) = 3 + (3 + 6t) e^{-2t} \text{ A}$$

Voltage across Capacitor is same as $V_L = L \frac{di(t)}{dt}$


then $V(t) = 5 \left[-2(3 + 6t) e^{-2t} + 6 e^{-2t} \right]$

$$= 5 \left[\cancel{6(1 - 2t)} e^{-2t} \right]$$

$$= 5 \left[\cancel{-6 e^{-2t}} - 12t e^{-2t} + \cancel{6 e^{-2t}} \right]$$

$$V(t) = -60t e^{-2t} \text{ V} \quad \text{--- (2)}$$


Q4 (a)

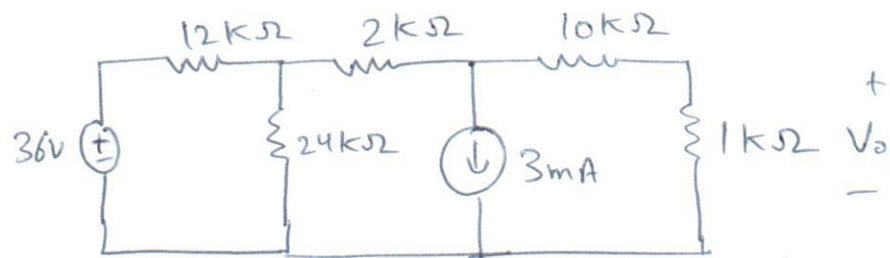

Use Norton's Theorem to find V_o ?

Solⁿ


R_N

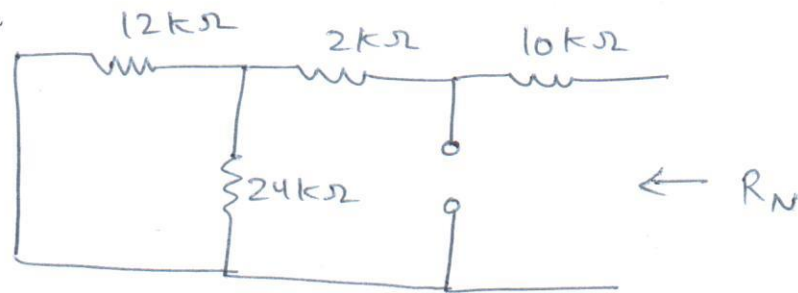


$$R_N = 10 + 2 + (12 \parallel 24) = 12 + 8 = 20 \text{ k}\Omega$$

1 mark


I_N

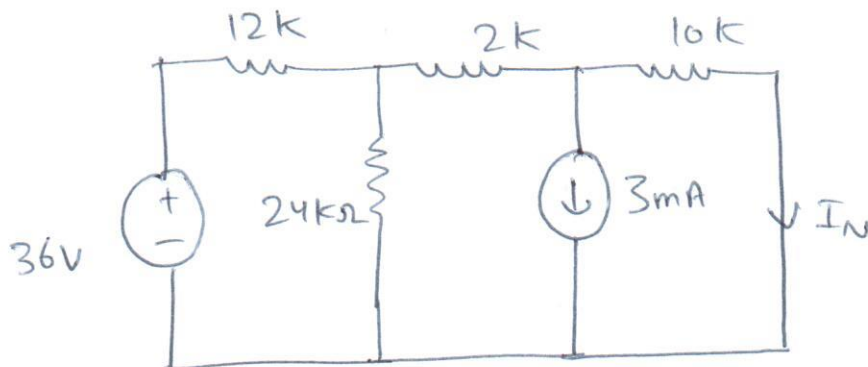

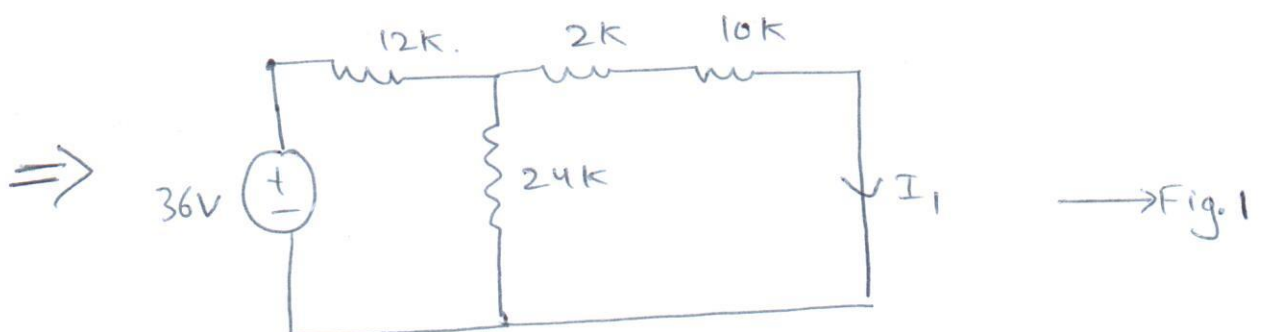• We can use Superposition theorem to find I_N .



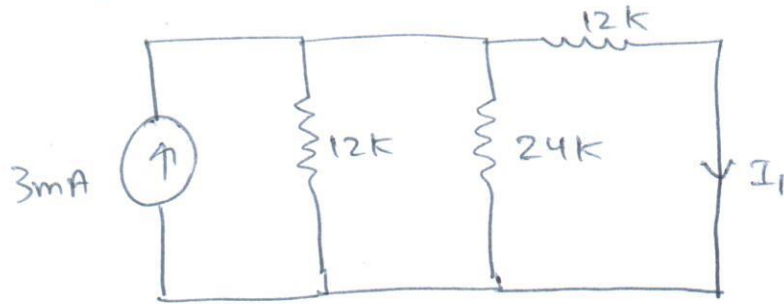
- Using Source transformation in Fig. 1, we get



- Using the Current division rule

$$I_1 = \frac{8}{8+12} \times (3\text{mA}) = 1.2\text{mA} \quad \text{--- (1)}$$

\Rightarrow

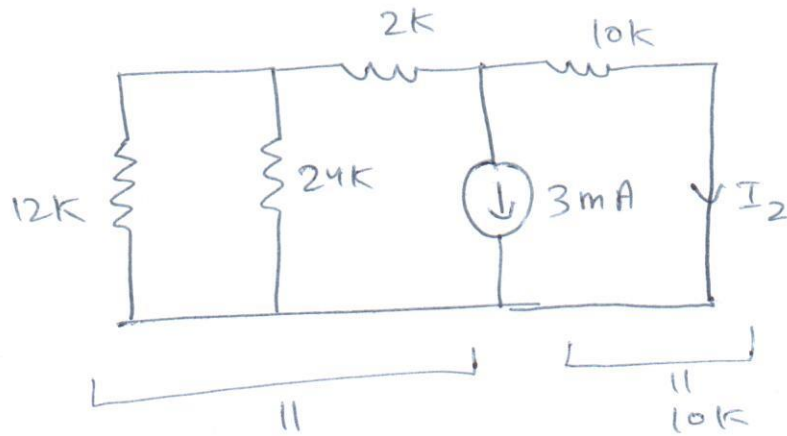

$$2\text{k} + (12\text{k} || 24\text{k}) = 10\text{k}$$

- Again applying Current division

$$I_2 = -1.5\text{mA}$$


$$\therefore I_N = I_1 + I_2 = 1.2 - 1.5$$

$$I_N = -0.3\text{mA}$$

2 marks.

- The Norton Equivalent Circuit will be

(2)

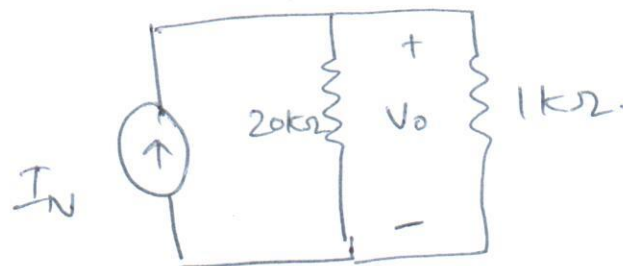


$$V_o = 1k \cdot \left[\frac{20}{20+1} \right] (-0.3 \text{ mA})$$

$$V_o = -285.7 \text{ mV} \quad \underline{\underline{\text{Ans}}}$$

1 mark

Q4 (b)

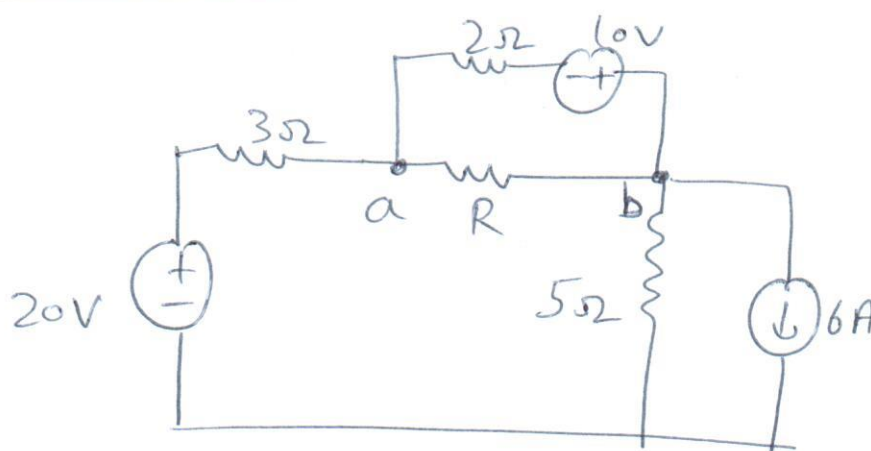


Find max. power that can be delivered to 'R'.

Solu

- We first find the Thevenin Equivalent at 'a' and 'b'


R_{th}

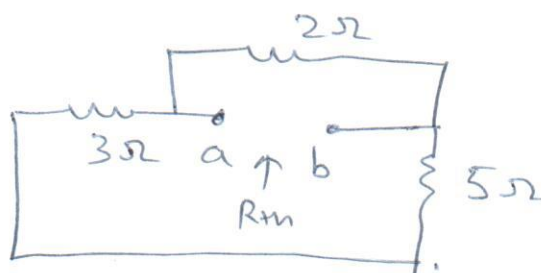

$$R_{th} = 2 \parallel (3+5) = 1.6$$

'1 mark'

V_{th}

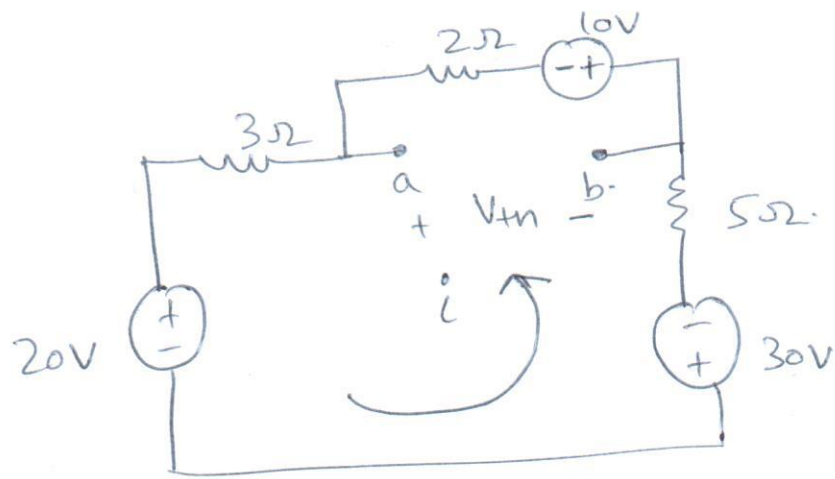

} Obtained by
doing source
transformation

$$\bullet \quad 10i + 30 + 10 + 20 = 0$$

$$i = -6$$

$$\bullet \quad V_{th} + 10 + 2i = 0$$

$$V_{th} = 2V$$

1 mark

$$\bullet \quad \text{For maximum power transfer} \quad R = R_{th}$$

$$\text{Max. power} = \frac{V_{th}^2}{4R_{th}}$$

$$= \frac{(2)^2}{4(1.6)} = 625 \text{ mW} \quad \underline{\text{Ans}}$$

2 marks