

# ELECTRONICS - I

## END TERM SOLUTIONS.

11.

1) If  $V_o = +V_{cc} = +10V$ .

$$V_i = V_n = V_p$$

KCL at  $V_p$ .

$$\frac{V_p - 0}{R_1} + \frac{V_p - 10}{R_2} = 0$$

$$V_p \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{10}{R_2} \Rightarrow V_p = \frac{10R_1}{R_1 + R_2}$$

$$\Rightarrow V_i = \frac{10 \times 2}{6} = \frac{10}{3} V$$

Similarly for  $V_o = -V_{cc} = -10V$   $V_i = -\frac{10}{3} V$

For  $V_o = 10V = +V_{cc}$ .

KCL at  $V_p$ .

$$\frac{V_p - 2}{R_1} + \frac{V_p - 10}{R_2} = 0$$



$$V_p \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{2}{R_1} + \frac{10}{R_2}$$

$$\Rightarrow V_p = V_i = \left( \frac{2}{R_1} + \frac{10}{R_2} \right) \frac{R_1 R_2}{R_1 + R_2} = \left( \frac{2}{2} + \frac{10}{4} \right) \frac{8}{6} = +\frac{14}{3} V$$

for  $V_o = -10V$ .

$$\frac{V_p - 2}{R_1} + \frac{V_p + 10}{R_2} = 0 \Rightarrow V_i =$$
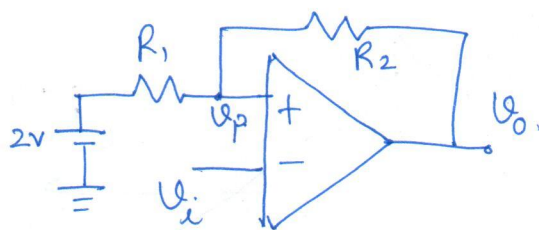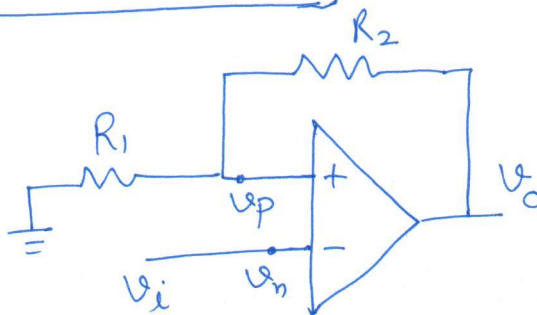
$$V_p \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{2}{R_1} - \frac{10}{R_2} \Rightarrow V_p = \left( \frac{2}{2} - \frac{10}{4} \right) \times \frac{2 \times 4}{2+4} = -\frac{6}{3} = -2V$$



3


2)

$$\frac{2000 (j\omega + 0.5)}{j\omega (j\omega + 10) (j\omega + 50)}$$


$$= \frac{2000 \times \frac{1}{2} \left( \frac{j\omega}{0.5} + 1 \right)}{j\omega \times 10 \left( \frac{j\omega}{10} + 1 \right) \times 50 \left( \frac{j\omega}{50} + 1 \right)}$$

$$= \frac{2 \left( \frac{j\omega}{0.5} + 1 \right)}{j\omega \left( \frac{j\omega}{10} + 1 \right) \left( \frac{j\omega}{50} + 1 \right)}$$


∴ Individual plots are.

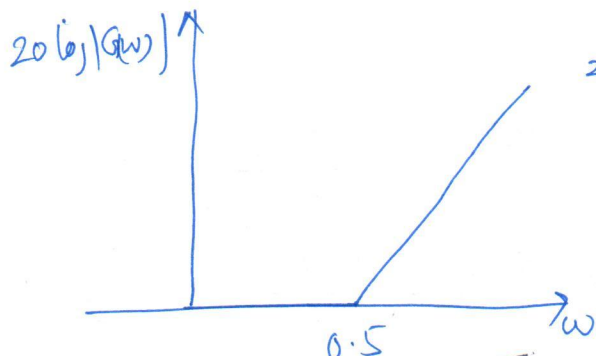

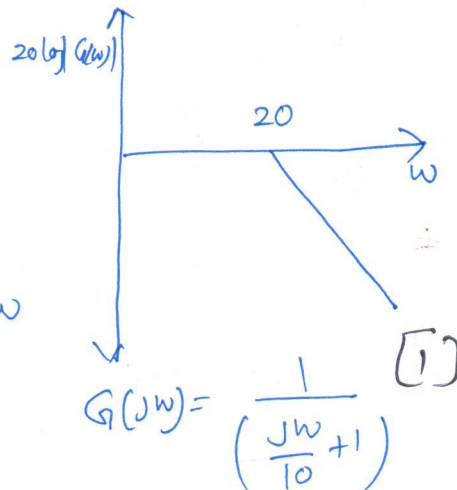
$$G(j\omega) = \left( \frac{j\omega}{0.5} + 1 \right) \quad [1]$$


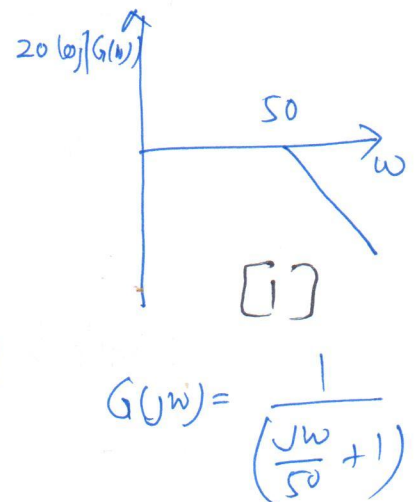
$$G(j\omega) = \frac{1}{\left( \frac{j\omega}{10} + 1 \right)} \quad [1]$$



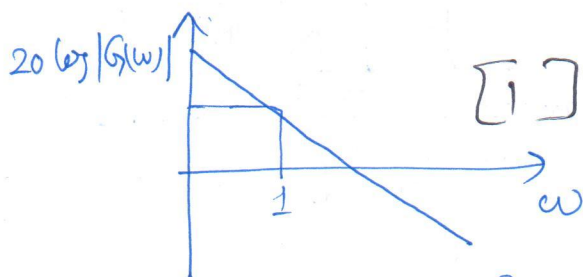
$$G(j\omega) = \frac{1}{\left( \frac{j\omega}{50} + 1 \right)}$$



$$G(j\omega) = \frac{2}{j\omega}$$

∴ Total Graph.

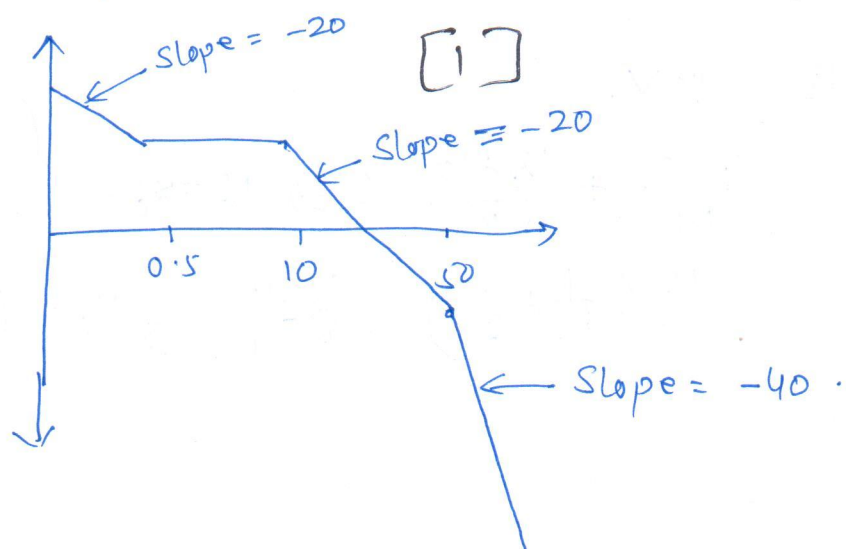

3)

Delay of flip flop =  $T_{prop} + T_{setup} + T_{hold}$ .

$\therefore$  Min delay of FF =  $4 + 5 + 1 = 10 \text{ ns}$

Max " " " =  $7 + 5 + 1 = 13$  ns.

Delay of logic gate =  $T_{prop}$ .

$\therefore$  Min delay of gate = 2ns, Max delay = 6ns.

In path from A to V, output is dependent of P and Q.

$\therefore$  Total of 3 gates and 2 FF. [1]

Hex gate 1 and FF C1 are in parallel. So the component with larger delay would be considered.

$$\begin{aligned} T_{A-v} \min &= 2 \times 10 + 3 \times 2 = 26 \text{ ns} \\ T_{A-v} \max &= 2 \times 13 + 3 \times 6 = 44 \text{ ns} \end{aligned} \quad \Bigg] \text{ [6]}$$

$$T_{A-v} \text{ max} = 2 \times 18 + 3 \times 6 = 44 \text{ ns}$$

Similarly for B to V. 2 FF and 3 gates. [1]

$$\begin{aligned} T_{B-V} \text{ min} &= 2 \times 10 + 3 \times 2 = 26 \text{ ns} \\ T_{B-V} \text{ max} &= 2 \times 13 + 3 \times 6 = 44 \text{ ns} \end{aligned} \quad ] [ ]$$

$$T_{B-V} \text{ max} = 2 \times 13 + 3 \times 6 = 44 \text{ ms}$$

For max clock frequency, we need minimum delay.

$$f_{\max} = \frac{1}{T_{\min}} = \frac{1}{26 \text{ ns}} = 38.46 \text{ MHz} \quad [1]$$

$$4) V_p = \left( \frac{R/3}{R + \frac{R}{3}} \right) V_2 + \left( \frac{R/3}{R + \frac{R}{3}} \right) V_4 + \left( \frac{R/3}{R + \frac{R}{3}} \right) V_6$$


$$= \frac{1}{4} (u_2 + u_4 + u_6)$$

KCL at  $V_n$  and put  $V_p = V_n$  (3)

$$\frac{U_p - U_1}{R} + \frac{U_p - U_3}{R} + \frac{U_p - U_5}{R} + \frac{U_p - U_0}{R} = 0$$

$$V_0 = 4V_p - (V_1 + V_3 + V_5)$$
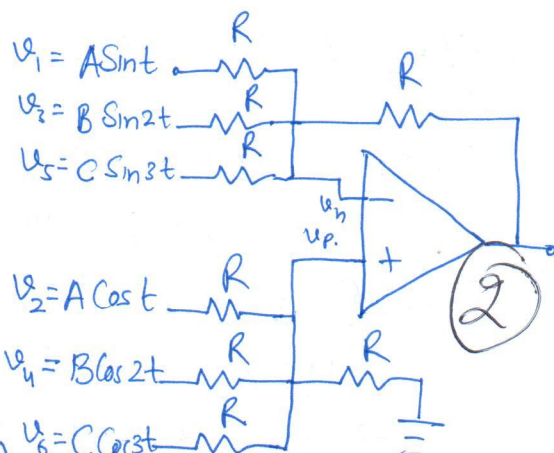
$$= (u_2 - u_1) + (u_4 - u_3) + (u_6 - u_5)$$



5). Considering only 1mA source.

$$I_1 = 1 \text{ mA}$$

KVL in loop 1




$$4x1 + 7(1 - I_2) = 0 \quad \text{--- (i)}$$

KVL in loop 2.

$$5I_2 + \frac{48}{14}I_2 + 7(I_2 - I_1) = 0 \quad \text{--- (ii)}$$

$$4 + 7 - 7I_2 = 0$$

$$I_2 = \frac{11}{7} \text{ mA}$$

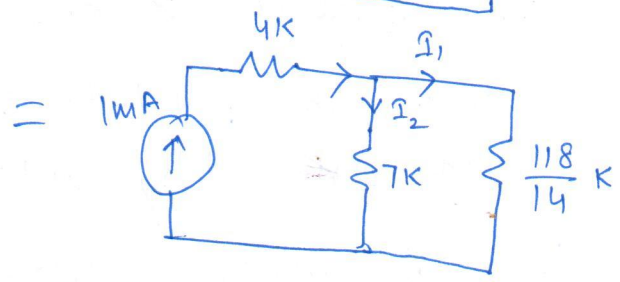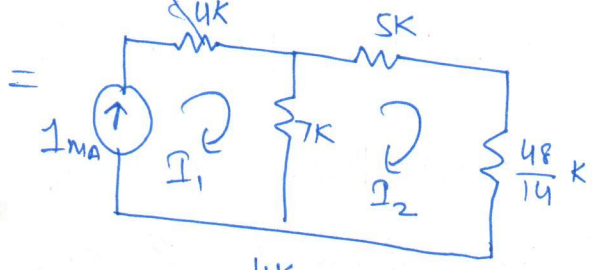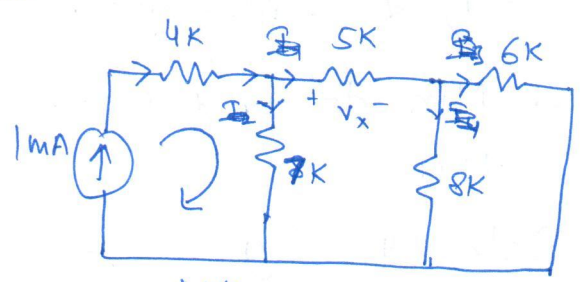

$$I_1 = \frac{1 \text{ mA} \times 7 \text{ k}}{7 \text{ k} + \frac{118}{14} \text{ k}} = \frac{7 \times 14}{216} = 0.45 \text{ mA}$$

$$\therefore V_{x1} = I_1 \times 5 \text{ k}\Omega = 2.26 \text{ V} \quad \checkmark$$


$\Rightarrow$  Considering only 2V source.

KCL at X.

$$\frac{X-0}{8} + \frac{X+2-0}{6} + \frac{X+2-Y}{5} = 0$$

$$15X + 20X + 40 + 24X + 48 - 24Y = 0$$

$$59X - 24Y = -88 \quad \text{--- (i)}$$

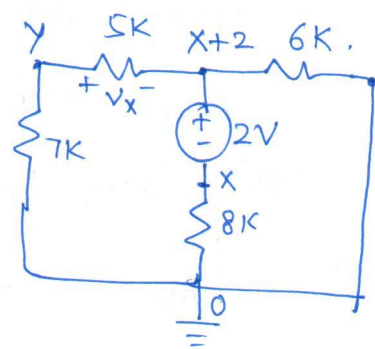

KCL at Y.

$$\frac{0-Y}{7} + \frac{X+2-Y}{5} = 0$$

$$-5Y + 7X + 14 - 7Y = 0$$

$$7X - 12Y = -14 \quad \text{--- (ii)}$$

$$\textcircled{i} - 2\textcircled{ii} \Rightarrow$$

$$45X = -60 \Rightarrow X = -\frac{4}{3} \quad \checkmark$$

$$\Rightarrow Y = \frac{7(-\frac{4}{3}) + 14}{12} = \frac{14}{36} \therefore V_X = Y - (X+2)$$

$$(V_{X2} = -0.277 \text{ V})$$


$$\frac{14}{36} + \frac{4}{3} - 2 = -\frac{10}{36}$$

(3)



Considering only 3V source.

15

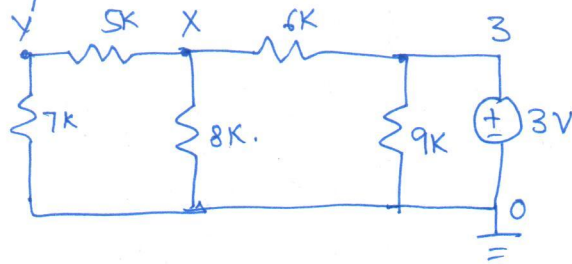

KCL at X:  $\frac{X-3}{6} + \frac{X-0}{8} + \frac{X-Y}{5} = 0$

$$20X - 60 + 15X + 24X - 24Y = 0$$

$$59X - 24Y = 60 \quad \text{--- (I)}$$

KCL at Y:  $\frac{0-Y}{7} + \frac{X-Y}{5} = 0$

$$-5Y + 7X - 7Y = 0$$

$$7X - 12Y = 0 \quad \text{--- (II)}$$

$$\textcircled{I} - 2\textcircled{II} \Rightarrow$$

$$45X = 60 \Rightarrow X = \frac{4}{3}$$

$$Y = \frac{7 \times \frac{4}{3}}{12} = \frac{28}{36} = \frac{7}{9}$$

$$\therefore V_{X3} = Y - X = \frac{7}{9} - \frac{4}{3} = \frac{7-12}{9} = -\frac{5}{9}$$


$$\textcircled{2} = -0.55 \text{ V}$$

$$\therefore \text{Total } V_X = 2.26 - 0.277 - 0.55 = 1.42 \text{ V}$$


6)

$X_2 X_1 X_0$	$Y_2 Y_1 Y_0$
000	011
001	100
010	101
011	000
100	001
101	011
110	011
111	100


$\textcircled{2}$

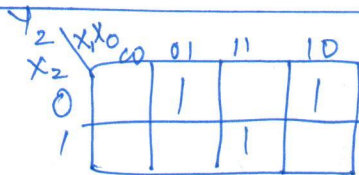
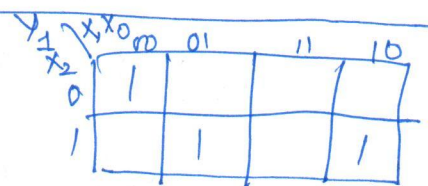
$$Y_2 = \bar{X}_2 \bar{X}_1 X_0 + \bar{X}_2 X_1 \bar{X}_0 + X_2 X_1 X_0$$


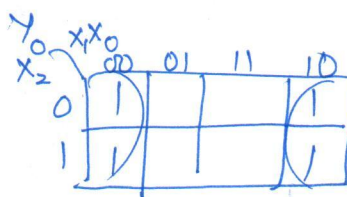
$$Y_1 = \bar{X}_2 \bar{X}_1 \bar{X}_0 + X_2 \bar{X}_1 X_0 + X_2 X_1 \bar{X}_0$$




$$Y_0 = \bar{X}_0$$

$\textcircled{2}$

∴ Combinational ckt is

6

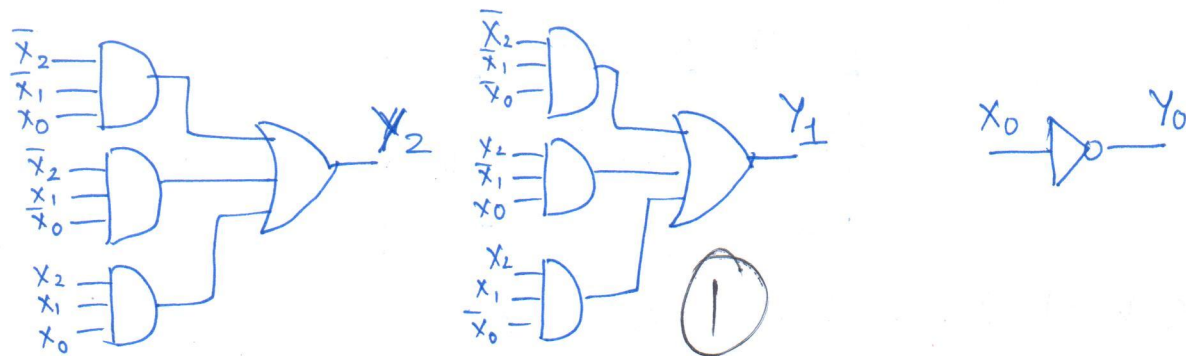

7) In characteristics table 3 input variables A, B, C along with  $Q(t)$  would decide  $Q(t+1)$ .

A	B	C	$Q(t)$	$Q(t+1)$
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		$Q(t+1)$			
		$C Q(t)$			
A-B		00	01	11	10
		0	1	0	0
00		0	1	0	0
01		0	0	1	1
11		0	0	1	1
10		1	1	0	1

$$Q(t+1) = BC + A\bar{B}\bar{Q}(t) + \bar{B}\bar{C}Q(t)$$

Excitation Table.

$Q(t)$	$Q(t+1)$	A	B	C
0	0	x	x	x
0	1	x	x	x
1	0	x	x	x
1	1	x	x	x



10)

With Shift = 1

With Shift = 0

8

$X_3 X_2 X_1 X_0$	$Y_3 Y_2 Y_1 Y_0$	$Y_3 Y_2 Y_1 Y_0$
0 0 0 0	0 0 0 0	0 0 0 0
0 0 0 1	0 0 1 0	0 0 0 1
0 0 1 0	0 1 0 0	0 0 1 0
0 0 1 1	0 1 1 0	0 0 1 1
0 1 0 0	1 0 0 0	0 1 0 0
0 1 0 1	1 0 1 0	0 1 0 1
0 1 1 0	1 1 0 0	0 1 1 0
0 1 1 1	1 1 1 0	0 1 1 1
1 0 0 0	0 0 0 0	1 0 0 0
1 0 0 1	0 0 1 0	1 0 0 1
1 0 1 0	0 1 0 0	1 0 1 0
1 0 1 1	0 1 1 0	1 0 1 1
1 1 0 0	1 0 0 0	1 1 0 0
1 1 0 1	1 0 1 0	1 1 0 1
1 1 1 0	1 1 0 0	1 1 1 0
1 1 1 1	1 1 1 0	1 1 1 1

[2]

[1]

∴ The circuit doesn't do anything if Shift = 0.

and It shift X towards left by 1 bit by replacing  
LSB with 0 and excluding the overflown MSB.

[2]

∴ It is a left shifter.