

Time: 180 Minutes

Maximum Marks: 100

Student's roll number:

Student's name:

**Important Notes:** This question paper consists of **two** sections having six questions in each, that is, total twelve questions. **Five** questions from each section are required to be answered. All questions carry equal marks.

**Section I**

1. A 10-bit binary data 0011101101 is received, check using even parity Hamming code i). if received data is correct, ii). if there is an error determine the bit position and determine the corrected code and the uncoded message. Leftmost is the starting bit. [05]

$$\text{Total bits} = 10 = 4 \text{ parity bits} + 6 \text{ message bits}$$

P <sub>1</sub>	P <sub>2</sub>	M <sub>0</sub>	P <sub>4</sub>	M <sub>1</sub>	M <sub>2</sub>	M <sub>3</sub>	P <sub>8</sub>	M <sub>4</sub>	M <sub>5</sub>
0	0	1	1	1	0	1	1	0	1

(1)

Check if data received correctly:-

$$\begin{aligned} \text{Check for } P_1 &\Rightarrow 0 \oplus 1 \oplus 1 \oplus 1 \oplus 0 = 1 \\ \text{" " } P_2 &\Rightarrow 0 \oplus 1 \oplus 0 \oplus 1 \oplus 1 = 1 \\ \text{" " } P_4 &\Rightarrow 1 \oplus 1 \oplus 0 \oplus 1 = 1 \\ \text{" " } P_8 &= 1 \oplus 0 \oplus 1 = 0 \end{aligned} \quad \left. \begin{array}{l} \text{(To make it even)} \\ \text{Shows error in} \\ \text{received data} \end{array} \right\}$$

(2)

$$\text{Sum of } P_1 + P_2 + P_4 + P_8 = 1 + 2 + 4 = 7$$

bit position from left 7 has error i.e.  $m_3 = 1 \rightarrow 0$


Correct code is :- 0011100101 (1)

and uncoded message - 110001 (1)




2. Draw the multi-level NOR and multi-level NAND circuits for the expression:  $(AB' + CD')E + BC(A + B)$ .


[05]

 

NOR implementations:-

 

NAND implementations:-

 

3. Show that the dual of the EX-NOR is equal to EX-OR and show also, using truth table, that a positive logic NAND gate is a negative logic NOR gate.

[05]

Dual of EX-NOR:-  
assuming inputs  $x$  &  $y$ , then

$$\text{EX-NOR} \Rightarrow x \odot y = x \cdot y + x' \cdot y'$$

$$\begin{aligned} \text{dual of it :-} &= (x+y) \cdot (x'+y') = xx' + xy' + x'y + yy' \\ &= xy' + x'y = x \oplus y = \underline{\text{EX-OR}} \end{aligned}$$

Assuming a truth table for a gate having two i/p's  $x$  &  $y$  (and) o/p  $z$ :-

$x$	$y$	$z$
L	L	H
L	H	H
H	L	H
H	H	L

①

Positive logic for this table

$x$	$y$	$z$
0	0	1 $\rightarrow$ H
0	1	1 $\rightarrow$ H
1	0	1 $\rightarrow$ H
1	1	0 $\rightarrow$ L

①  $\rightarrow$  This is a NAND gate  
o/p (+ve logic)

-ve logic for this table

$x$	$y$	$z$
1	1	0 $\rightarrow$ H
1	0	0 $\rightarrow$ H
0	1	0 $\rightarrow$ H
0	0	1 $\rightarrow$ L


①  $\rightarrow$  This is a NOR gate o/p  
(-ve logic)

4. Construct a JK flip-flop using a D flip-flop a two-to-one line multiplexer and an inverter.

[05]

Relationship bet<sup>n</sup> D & JK  $\Rightarrow D = JQ' + K'Q$


to implement this:-

 




5. Construct an eight-to-one line multiplexer using transmission gates and inverters.

[05]

 

6. Find the output timing diagram for the circuit shown in the following figure:

[05]

 

Non-overlapping clock pulses:-

Student's roll number:


Student's name:

**Important Notes:** This question paper consists of two sections having six questions in each, that is, total twelve questions. Five questions from each section are required to be answered. All questions carry equal marks.



## Section II

1. Find the output voltage  $V_{out}$  under steady state for the circuit shown in the following figure, where all nodes are discharged to 0V, except the output node  $V_{out}$  which is pre-charged at 5 Volts ( $|V_{th,p}| = V_{th,p} = 1V$ ).

[05]

 

Initial Condition:

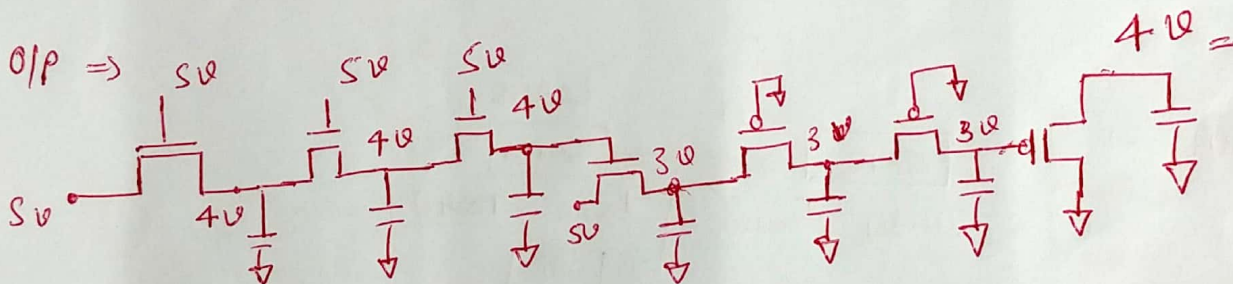 


$$\boxed{O/P = 4V \text{ Ans}}$$



2. (a) Find **Fanout** (input and output) and **Noise Margin** (upper and lower) for TTL series logic gates with following ratings:

Max. voltage for logic '0' at i/p =  $V_{IL,max} = 2.5$  V, Max. voltage for logic '0' at o/p =  $V_{OL,max} = 2.8$  V,  
 Min. voltage for logic '1' at i/p =  $V_{IH,min} = 2.0$  V, Min. voltage for logic '1' at o/p =  $V_{OH,min} = 0.7$  V  
 Max. sourcing current from the i/p of a logic gate = 0.1 mA,  
 Max. sinking current into the i/p of a logic gate = 10  $\mu$ A,  
 Max. sourcing current from the o/p of a logic gate = 400  $\mu$ A,  
 Max. sinking current into the o/p of a logic gate = 8 mA.

[05]

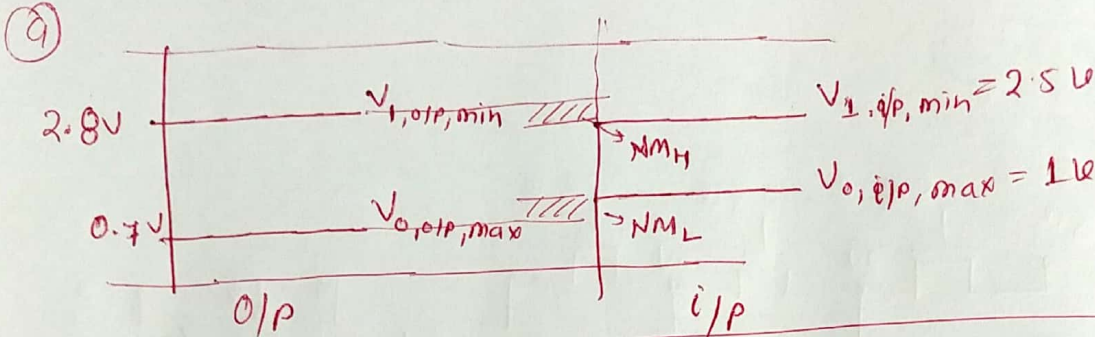


$$NM_H = 2.8 - 2.5 = 0.3 \text{ V}$$

$$NM_L = 2.5 - 2.0 = 0.5 \text{ V}$$


Ans.

- (b) fanout  $\rightarrow$

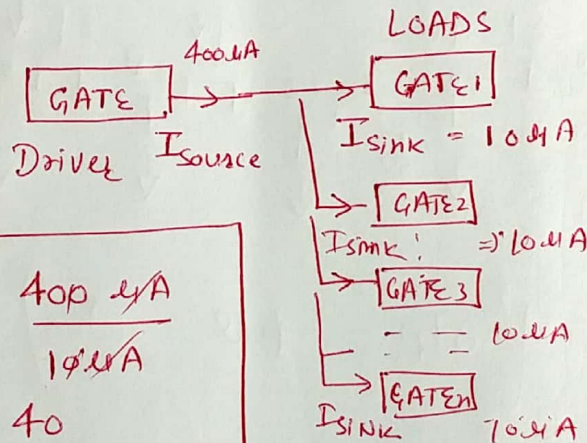

$$FANOUT_1 = \frac{400 \mu A}{10 \mu A} = 40$$

Ans

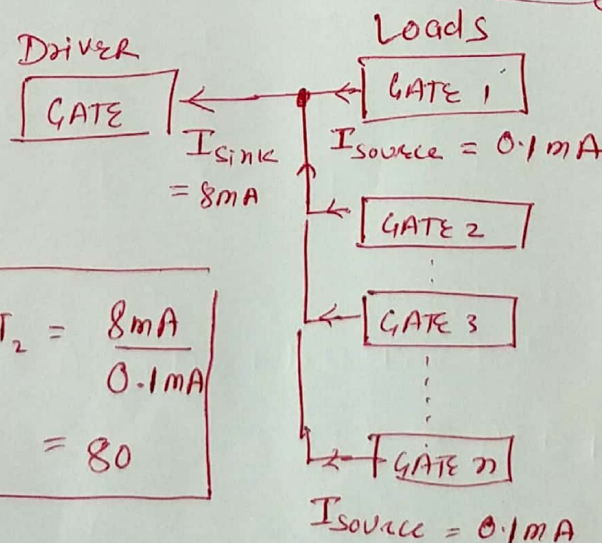

$$FANOUT_2 = \frac{8 \text{ mA}}{0.1 \text{ mA}} = 80$$



Ans

3. Design a memory cell for circuit shown in the following figure with following functions: - The memory cell 1 should select when  $Sel = '1'$ , The memory cell 2 should select when  $Sel = '0'$ .

**Operation:** When a memory cell is selected, with  $RD'/WR = '0'$  the content of the respective memory cell must transfer to the "Content Read Line", and when  $RD'/WR = '1'$  the content of the "Content Write Line" transferred into the respective memory cell.

Use logic gates and D-FFs to implement the memory cell.

[05]

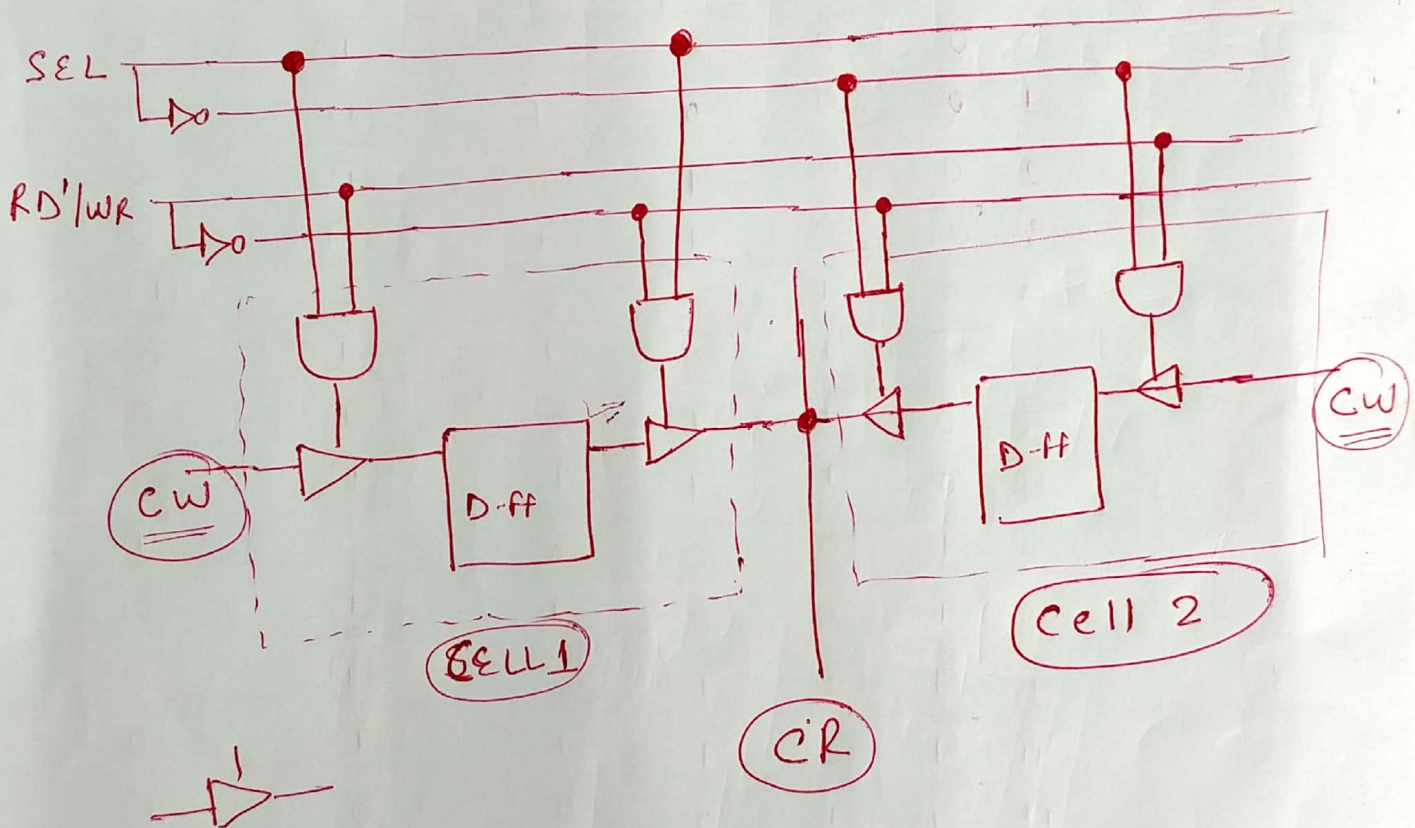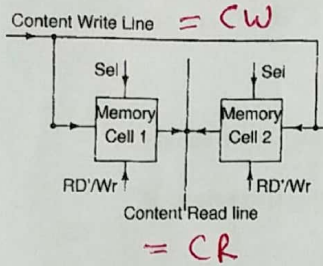

Tristate Buffer





4. The following figure shows the intersection of a main highway with a secondary access road. Vehicle detection sensors are placed along lanes C and D (main road) and lanes A and B (access road). These sensor outputs are low (0) when no vehicle is present and High (1) when a vehicle is present. The intersection traffic light is to be controlled according to the following logic:

- (1). The east-west (E-W) traffic light will be green whenever **both** lanes C and D are occupied.
- (2). The E-W light will be green whenever **either** C or D is occupied **but** lanes A and B are not **both** occupied.
- (3). The north-south (N-S) light will be green whenever **both** lanes A and B are occupied **but** C and D are not **both** occupied.
- (4). The N-S will also be green when **either** A or B is occupied while C and D are **both** vacant.
- (5). The E-W light will be green when **no** vehicle are present.

Using the sensor outputs A, B, C, and D as inputs, design a logic circuit to control the traffic light. There should be two outputs, N-S and E-W, that go high when the corresponding light is to be green.

\*\*\* use your rough sheets for analysis and write **ONLY** the truth table and Boolean expression of outputs N-S and E-W as a function of A, B, C, and D in main answer sheet.

[05]

  

	A	B	C	D	E-W	N-S
0	0	0	0	0	1	0
1	0	0	0	1	1	0
2	0	0	1	0	1	0
3	0	0	1	1	1	0
4	0	1	0	0	0	1
5	0	1	0	1	1	0
6	0	1	1	0	1	0
7	0	1	1	1	1	0
8	1	0	0	0	0	1
9	1	0	0	1	1	0
10	1	0	1	0	1	0
11	1	0	1	1	1	0
12	1	1	0	0	0	1
13	1	1	0	1	0	1
14	1	1	1	0	<del>0</del>	1
15	1	1	1	1	1	0

$$E-W = \sum (0, 1, 2, 3, 5, 6, 7, 9, 10, 11, 15)$$

$$= A'B' + A'D + B'D + A'C + B'C + CD$$

$$N-S = \sum (4, 8, 12, 13, 14) = AB\bar{D} + ABC' + AC'D' + BC'D'$$


$$\boxed{E-W \text{ OR } N-S = '1' \text{ for "Verification"}}$$



 
5. Design a circuit (for the following figure) with input a square wave signal with fundamental frequency  $f_{clk}$  that produces another square wave signal with fundamental frequency  $f_{clk}/6$  as output.

[05]

Hint: A square wave signal has 50% duty cycle.



Johnson Counter with 3 stages

 

CLR ⇒ "is not must"


000
100
110
111
011
001
000

Repeat

100

6. Design expression  $Y = [A'BC + B'C + C']'$  with (a) Minimum number of MOS transistors (use PMOS and/or NMOS to implement) (b) Static CMOS logic. [05]

(a)

 


$$Y = \underline{ABC}$$

(after simplification)

"4 transistors"

(b)

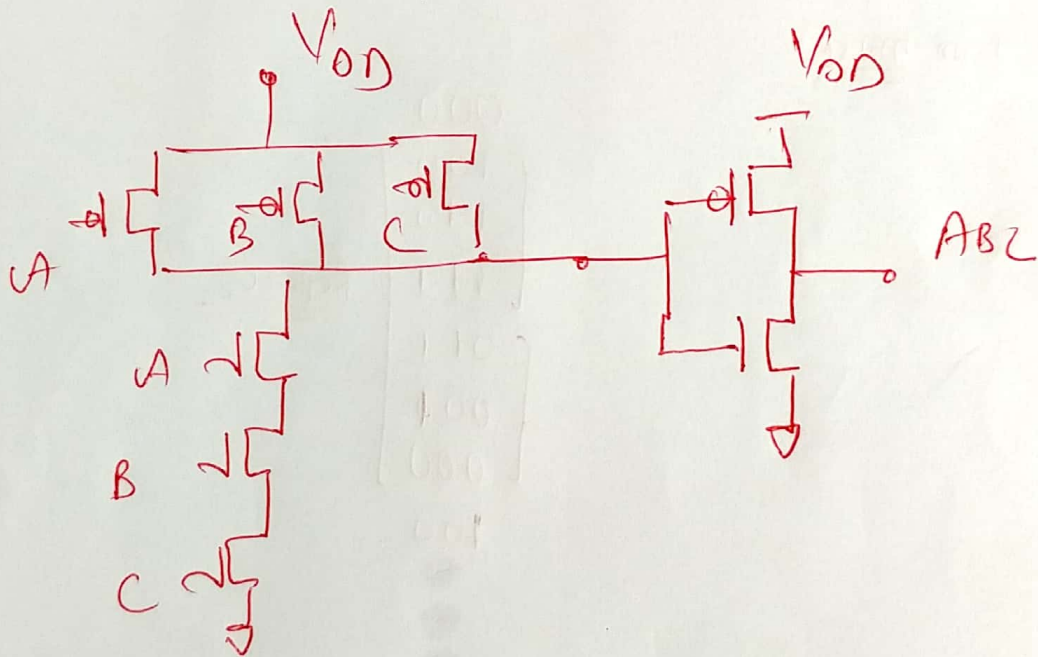

"8 transistors"